


Module 3: Assignment, Bandgap Circuit Design

Name: Anil Kumar,

B. Tech: 4th Yr, Student (ECE), NIET Greater, Noida

Email: anilkumar945798@gmail.com

Bandgap Circuit:

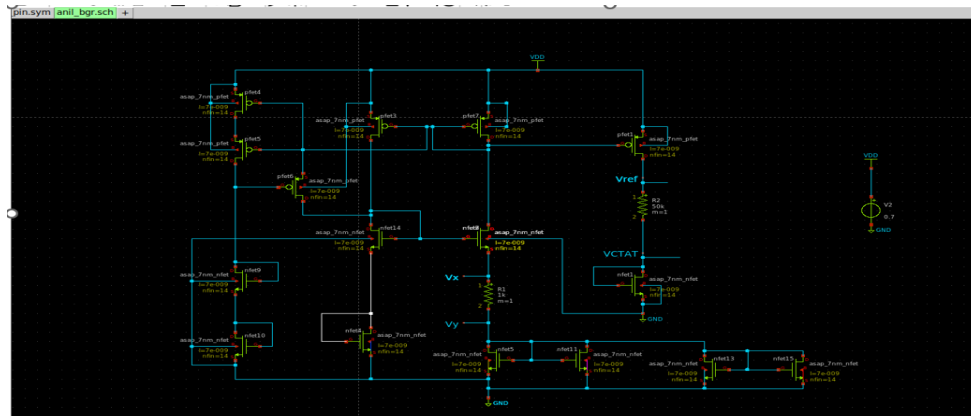

Generated Netlist and log. -

```
anil_bgr_ckt.spice (-~/Desktop/Bandgap-Reference-Circuit)
File Edit Tools Syntax Buffers Window Help
** sch_path: /home/vsduser/Desktop/Bandgap-Reference-Circuit-with-SCMB-with-ASAP-7nm-PDK-/anil_bgr.sch
** subckt anil_bgr
Xpfet1 Vref net1 VDD VDD asap_7nm_pfet l=7e-009 nfin=14
Xnfet1 VCTAT VCTAT GND asap_7nm_nfet l=7e-009 nfin=14
V2 VDD GND 0.7
Xpfet3 net4 net1 VDD VDD asap_7nm_pfet l=7e-009 nfin=14
Xpfet4 net2 net1 VDD VDD asap_7nm_pfet l=7e-009 nfin=14
Xpfet5 net3 net1 net2 VDD asap_7nm_pfet l=7e-009 nfin=14
Xpfet6 net4 net3 net1 VDD asap_7nm_pfet l=7e-009 nfin=14
Xnfet4 net6 net6 GND net5 asap_7nm_nfet l=7e-009 nfin=14
Xnfet5 Vy Vy GND net8 asap_7nm_nfet l=7e-009 nfin=14
Xpfet7 net1 net1 VDD VDD asap_7nm_pfet l=7e-009 nfin=14
R1 Vx Vy 1k m=1
R2 Vref VCTAT 50k m=1
Xnfet9 net3 net3 net7 GND asap_7nm_nfet l=7e-009 nfin=14
Xnfet10 net7 net7 GND GND asap_7nm_nfet l=7e-009 nfin=14
Xnfet11 Vy Vy GND net9 asap_7nm_nfet l=7e-009 nfin=14
Xnfet14 net4 net4 net6 GND asap_7nm_nfet l=7e-009 nfin=14
Xnfet13 Vy Vy GND GND asap_7nm_nfet l=7e-009 nfin=14
Xnfet15 Vy Vy GND net10 asap_7nm_nfet l=7e-009 nfin=14
Xnfet2 net1 net4 Vx GND asap_7nm_nfet l=7e-009 nfin=14
Xnfet3 net1 net4 Vx GND asap_7nm_nfet l=7e-009 nfin=14
Xnfet6 net1 net4 Vx GND asap_7nm_nfet l=7e-009 nfin=14
Xnfet7 net1 net4 Vx GND asap_7nm_nfet l=7e-009 nfin=14
**** begin user architecture code

.dc temp -40 150 5
.control
run
plot v(Vref)-v(VCTAT)
plot v(Vref)
plot v(VCTAT)
let temp_coff = deriv(V(Vref))*10e+06
plot temp_coff
plot abs(v2mbranch)
MEAS DC Vref_max MAX v(Vref)
MEAS DC Vref_min MIN v(Vref)
MEAS DC Vref_typ find v(Vref) at=27
let Delta_Vref = Vref_max-Vref_min
print Delta_Vref
```

```
Circuit: ** sch_path: /home/vsduser/desktop/bandgap-reference-circuit-with-SCMB-with-ASAP-7nm-PDK-/anil_bgr.sch



Warning: Model issue on line 58 :
.model bsimcng_osdi_p bsimcng_va ( type=0 version=107 bulkmod=1 igcm=1
unrecognized parameter (version) - ignored
unrecognized parameter (coremod) - ignored
unrecognized parameter (capmod) - ignored
unrecognized parameter (nseg) - ignored
unrecognized parameter (etaqm) - ignored

Warning: Model issue on line 133 :
.model bsimcng_osdi_n bsimcng_va ( type=1 version=107 bulkmod=1 igcm=1
unrecognized parameter (version) - ignored
unrecognized parameter (coremod) - ignored
unrecognized parameter (capmod) - ignored
unrecognized parameter (nseg) - ignored
unrecognized parameter (etaqm) - ignored

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Using SPARSE 1.3 as Direct Linear Solver
Note: Starting dynamic gmin stepping
Note: Dynamic gmin stepping completed
Reference value : 1.15000e+02
No. of Data Rows : 39
vref_max = 6.895768e-01 at= -4.000000e+01
vref_min = 6.879114e-01 at= 1.500000e+02
vref_typ = 6.892570e-01
delta_vref = 1.665400e-03
```

Resulting plot summary (VDD= 0.7V):

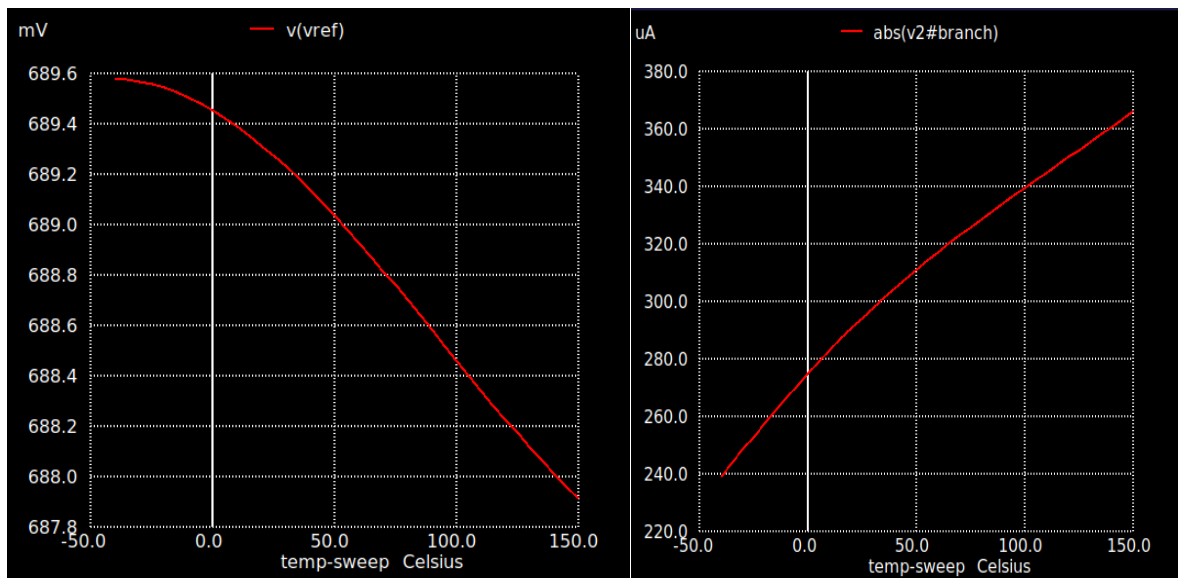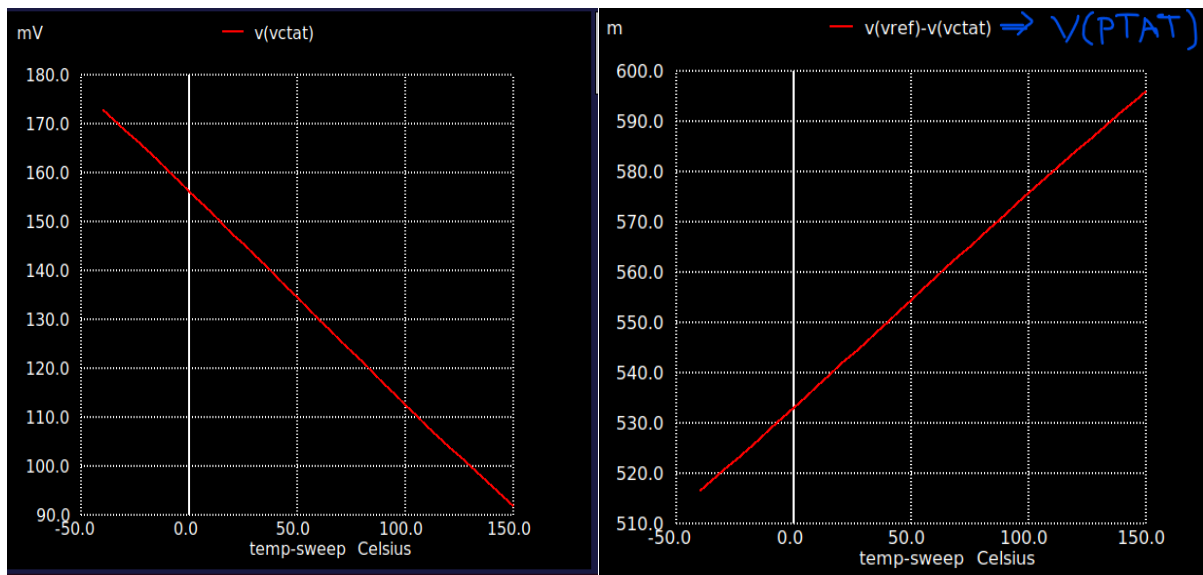

Generated logs:

VDD= 0.8V:

```
vref_max = 7.893026e-01 at= -4.000000e+01
vref_min = 7.873219e-01 at= 1.500000e+02
vref_typ = 7.887859e-01
vref_m40 = 7.893026e-01
vref_125 = 7.875827e-01
delta_vref = 1.980700e-03
```

VDD=0.9V:

```
No. of Data Rows : 39
vref_max = 8.889364e-01 at= -4.000000e+01
vref_min = 8.867492e-01 at= 1.500000e+02
vref_typ = 8.882370e-01
vref_m40 = 8.889364e-01
vref_125 = 8.870076e-01
delta_vref = 2.187200e-03
```

VDD=1V

```
No. of Data Rows : 39
vref_max = 9.885220e-01 at= -4.000000e+01
vref_min = 9.862060e-01 at= 1.500000e+02
vref_typ = 9.876875e-01
vref_m40 = 9.885220e-01
vref_125 = 9.864741e-01
delta_vref = 2.316800e-03
```

Results Summary:

Sr.	VDD (V)	Temp (°C)	Vref (V)
1	0.8	27	0.7887
2	0.9	27	0.8882
3	1	27	0.9876
4	1	-40	0.9885
5	1	125	0.9864

Line Regulation ($\Delta V_{ref}/\Delta V_{DD}$):

```
anil_bgr_ckt_LR.spice (-/Desktop/Bandg
File Edit Tools Syntax Buffers Window Help
** sch_path: /home/vsduser/Desktop/Bandgap-Reference-Circuit-with-SCMB-with-ASAP-7nm-PDK-/anil_bgr.sch
** subckt anil_bgr
Xpfet1 Vref net1 VDD VDD asap_7nm pfet l=7e-009 nfin=14
Xnfet1 VCTAT VCTAT GND GND asap_7nm nfet l=7e-009 nfin=14
V2 VDD GND 0.8
Xpfet3 net4 net1 VDD VDD asap_7nm pfet l=7e-009 nfin=14
Xpfet4 net2 net1 VDD VDD asap_7nm pfet l=7e-009 nfin=14
Xpfet5 net3 net1 net2 VDD VDD asap_7nm pfet l=7e-009 nfin=14
Xpfet6 net4 net3 net1 VDD asap_7nm pfet l=7e-009 nfin=14
Xnfet4 net6 net6 GND net5 asap_7nm nfet l=7e-009 nfin=14
Xnfet5 Vy Vy GND net8 asap_7nm nfet l=7e-009 nfin=14
Xpfet7 net1 net1 VDD VDD asap_7nm pfet l=7e-009 nfin=14
R1 Vx Vy 1k m=1
R2 Vref VCTAT 50k m=1
Xnfet9 net3 net3 net7 GND asap_7nm nfet l=7e-009 nfin=14
Xnfet10 net7 net7 GND GND asap_7nm nfet l=7e-009 nfin=14
Xnfet11 Vy Vy GND net9 asap_7nm nfet l=7e-009 nfin=14
Xnfet14 net4 net4 net6 GND asap_7nm nfet l=7e-009 nfin=14
Xnfet13 Vy Vy GND GND asap_7nm nfet l=7e-009 nfin=14
Xnfet15 Vy Vy GND net10 asap_7nm nfet l=7e-009 nfin=14
Xnfet2 net1 net4 Vx GND asap_7nm nfet l=7e-009 nfin=14
Xnfet3 net1 net4 Vx GND asap_7nm nfet l=7e-009 nfin=14
Xnfet6 net1 net4 Vx GND asap_7nm nfet l=7e-009 nfin=14
Xnfet7 net1 net4 Vx GND asap_7nm nfet l=7e-009 nfin=14
**** begin user architecture code
.dc V2 0.8 1 0
.temp 27
***.dc temp -40 150 5
.control
run
plot v(Vref)-v(VCTAT)
plot v(Vref)
plot v(VCTAT)
plot abs(v2#branch)
MEAS DC Vref_max MAX v(Vref)
MEAS DC Vref_min MIN v(Vref)
let Delta_Vref = Vref_max-Vref_min
print Delta_Vref
```

When Sweeping DC Supply VDD from 0.8V to 1V. ($\Delta V_{DD}=0.2$)

At temp 27C,

```
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
No. of Data Rows : 3
vref_max = 9.876871e-01 at= 1.000000e+00
vref_min = 7.887801e-01 at= 8.000000e-01
delta_vref = 1.989010e-01
```

→ $\Delta V_{ref}/\Delta V_{DD} = 0.1989/0.2 = 0.9945 = 994.5m$

When Sweeping DC Supply VDD from 0.8V to 1V. ($\Delta V_{DD}=0.2$)

At temp -40C,

```
Doing analysis at TEMP = -40.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Note: Starting dynamic gmin stepping
Note: Dynamic gmin stepping completed
No. of Data Rows : 3
vref_max = 9.885220e-01 at= 1.000000e+00
vref_min = 7.893026e-01 at= 8.000000e-01
delta_vref = 1.992194e-01
```

→ $\Delta V_{ref}/\Delta V_{DD} = 0.1992/0.2 = 0.996 = 996m$

At temp 125C,

```
Doing analysis at TEMP = 125.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
No. of Data Rows : 3
vref_max = 9.864738e-01 at= 1.000000e+00
vref_min = 7.875823e-01 at= 8.000000e-01
delta_vref = 1.988915e-01
```

→ $\Delta V_{ref}/\Delta V_{DD} = 0.19889/0.2 = 0.99445 = 994.45m$

Results Summary:				
Sr.	VDD (V)	Temp (°C)	Vref (V)	Line Reg. (mV/V)
1	0.8	27	0.7887	994.5
2	0.9	27	0.8882	994.5
3	1	27	0.9876	994.5
4	1	-40	0.9885	996
5	1	125	0.9864	994.45


TRAN simulation:

Generated Netlist:

```
anil_bgr_ckt_TRAN.spice + (-/Desktop/B
File Edit Tools Syntax Buffers Window Help
** sch_path: /home/vsduser/Desktop/Bandgap-Reference-Circuit-with-SCMB-with-ASAP-7nm-PDK-/anil_bgr.sch
** subckt anil_bgr
Xpfet1 Vref net1 VDD VDD asap_7nm pfet l=7e-009 nfin=14
Xnfet1 VCTAT VCTAT GND GND asap_7nm nfet l=7e-009 nfin=14
V2 VDD GND pwl(0 0 50n 0.7)
*V2 VDD GND 0.7
Xpfet3 net4 net1 VDD VDD asap_7nm pfet l=7e-009 nfin=14
Xpfet4 net2 net1 VDD VDD asap_7nm pfet l=7e-009 nfin=14
Xpfet5 net3 net1 net2 VDD VDD asap_7nm pfet l=7e-009 nfin=14
Xpfet6 net4 net3 net1 VDD asap_7nm pfet l=7e-009 nfin=14
Xnfet4 net6 net6 GND net5 asap_7nm nfet l=7e-009 nfin=14
Xnfet5 Vy Vy GND net8 asap_7nm nfet l=7e-009 nfin=14
Xpfet7 net1 net1 VDD VDD asap_7nm pfet l=7e-009 nfin=14
R1 Vx Vy 1k m=1
R2 Vref VCTAT 50k m=1
Xnfet9 net3 net3 net7 GND asap_7nm nfet l=7e-009 nfin=14
Xnfet10 net7 net7 GND GND asap_7nm nfet l=7e-009 nfin=14
Xnfet11 Vy Vy GND net9 asap_7nm nfet l=7e-009 nfin=14
Xnfet14 net4 net4 net6 GND asap_7nm nfet l=7e-009 nfin=14
Xnfet13 Vy Vy GND GND asap_7nm nfet l=7e-009 nfin=14
Xnfet15 Vy Vy GND net10 asap_7nm nfet l=7e-009 nfin=14
Xnfet2 net1 net4 Vx GND asap_7nm nfet l=7e-009 nfin=14
Xnfet3 net1 net4 Vx GND asap_7nm nfet l=7e-009 nfin=14
Xnfet6 net1 net4 Vx GND asap_7nm nfet l=7e-009 nfin=14
Xnfet7 net1 net4 Vx GND asap_7nm nfet l=7e-009 nfin=14
**** begin user architecture code
.tran 100p 2u 0
.temp 27
***.dc temp -40 150 5
.control
run
plot v(Vref)-v(VCTAT)
plot v(Vref)
plot v(VCTAT)
plot abs(v2#branch)
MEAS TRAN Vref_avg AVG v(Vref) From = 1.5u To =2u
MEAS TRAN Vref_final find v(Vref) at = 1.5u
**measuring Tstartup for within 1% tolerance band for final Vref
MEAS TRAN Ts_test WHEN v(Vref)= '0.996.892567e-01' RISE=1
let Tstartup =50n -Ts_test
print Tstartup
**measuring Tstartup for reaching 90% of Vref
*MEAS TRAN Ts_trt_test WHEN v(Vref)= '0.9*Vref final ' RISE=1
*MEAS TRAN T_startup2 WHEN v(Vref)= '0.9*6.892567e-01' FALL=1
*MEAS TRAN T_startup2 at v(Vref)= '0.9*6.892567e-01' RISE=1
****
```

```
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Initial Transient Solution
.....
Node Voltage
----
vref 0
net1 0
vdd 0
vctat 0
net4 0
net2 0
net3 0
net6 0
vy 0
net8 0
vx 0
net7 0
net9 0
net10 0
v2#branch 0
Reference value : 1.99475e-06
No. of Data Rows : 20011
vref_avg = 6.892567e-01 from= 1.500000e-06 to= 2.000000e-06
vref_final = 6.892567e-01
ts_test = 4.950578e-08
tstartup = 4.942200e-10
```

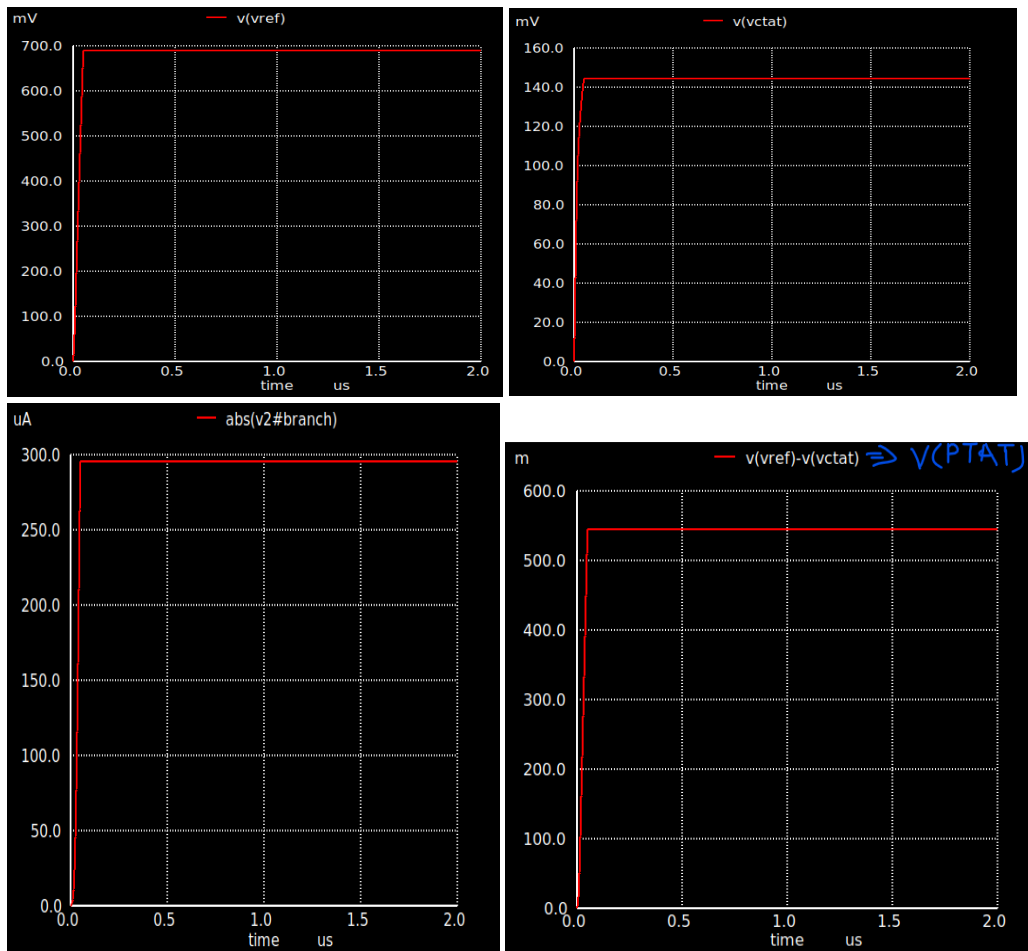Generated Plots- From above logs, **Tstartup** is 0.494ns.



When **VDD=0.8V**

```
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Initial Transient Solution
-----
Node      Voltage
----      -
vref      0
net1      0
vdd       0
vctat     0
net4      0
net2      0
net3      0
net6      0
net5      0
vy        0
net8      0
vx        0
net7      0
net9      0
net10     0
v2#branch 0
Reference value : 1.99255e-06
No. of Data Rows : 20011
vref_avg    = 7.887855e-01 from= 1.500000e-06 to= 2.000000e-06
vref_final  = 7.887855e-01
ts_test     = 4.950448e-08
tstartup    = 4.955280e-10
```

When **VDD=0.9V**

```
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Initial Transient Solution
-----
Node      Voltage
----      -
vref      0
net1      0
vdd       0
vctat     0
net4      0
net2      0
net3      0
net6      0
net5      0
vy        0
net8      0
vx        0
net7      0
net9      0
net10     0
v2#branch 0
Reference value : 1.99555e-06
No. of Data Rows : 20011
vref_avg    = 8.882367e-01 from= 1.500000e-06 to= 2.000000e-06
vref_final  = 8.882367e-01
ts_test     = 4.950378e-08
tstartup    = 4.962280e-10
```

VDD=1V, Temp =-40C

VDD=1V, Temp =125C

```

Doing analysis at TEMP = -40.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Initial Transient Solution
-----
Node          Voltage
----
vref          0
net1          0
vdd          0
vctat        0
net4          0
net2          0
net3          0
net6          0
net5          0
vy           0
net8          0
vx           0
net7          0
net9          0
net10         0
v2#branch     0

Reference value : 1.99665e-06
No. of Data Rows : 20011
vref_avg      = 9.885220e-01 from= 1.500000e-06 to= 2.000000e-06
vref_final    = 9.885220e-01
ts_test       = 4.950367e-08
tstartup      = 4.963300e-10

```

```

Doing analysis at TEMP = 125.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Initial Transient Solution
-----
Node          Voltage
----
vref          0
net1          0
vdd          0
vctat        0
net4          0
net2          0
net3          0
net6          0
net5          0
vy           0
net8          0
vx           0
net7          0
net9          0
net10         0
v2#branch     0

Reference value : 1.98905e-06
No. of Data Rows : 20011
vref_avg      = 9.864737e-01 from= 1.500000e-06 to= 2.000000e-06
vref_final    = 9.864737e-01
ts_test       = 4.950427e-08
tstartup      = 4.957300e-10

```

VDD=1V, temp= 27C

```


Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Initial Transient Solution
-----
Node          Voltage
----
vref          0
net1          0
vdd          0
vctat        0
net4          0
net2          0
net3          0
net6          0
net5          0
vy           0
net8          0
vx           0
net7          0
net9          0
net10         0
v2#branch     0

Reference value : 1.99405e-06
No. of Data Rows : 20011
vref_avg      = 9.876870e-01 from= 1.500000e-06 to= 2.000000e-06
vref_final    = 9.876870e-01
ts_test       = 4.950360e-08
tstartup      = 4.964000e-10

```

Results Summary:					
Sr.	VDD (V)	Temp (°C)	Vref (V)	Line Reg. (mV/V)	Startup Time (ns)
1	0.8	27	0.7887	994.5	0.495
2	0.9	27	0.8882	994.5	0.496
3	1	27	0.9876	994.5	0.4964
4	1	-40	0.9885	996	0.4963
5	1	125	0.9864	994.45	0.4957

Test Case with Vuniq Resistor:

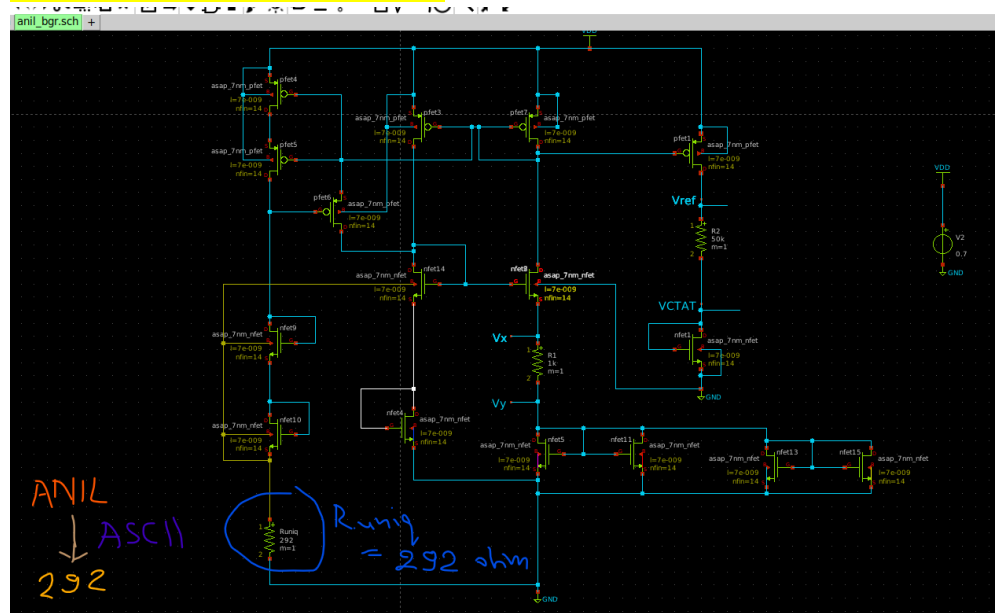

Generated Reports:

```

anil_bgr_ckt_TRAN.spice (~/Desktop/Bandgap-Ref
File Edit Tools Syntax Buffers Window Help
* sch path: /home/vsduser/Desktop/Bandgap-Reference-Circuit-with-SOMB-with-ASAP-7nm-PDK-/anil_bgr.sch
** subckt anil_bgr
Xpft1 Vref net1 VDD VDD asap_7nm_pft l=7e-009 nfin=14
Xnft1 VCTAT VCTAT GND GND asap_7nm_nft l=7e-009 nfin=14
V2 VDD GND pwl(0 0 50n 0.7)
*V2 VDD GND 0.7
Xpft3 net4 net1 VDD VDD asap_7nm_pft l=7e-009 nfin=14
Xpft4 net2 net1 VDD VDD asap_7nm_pft l=7e-009 nfin=14
Xpft5 net3 net1 net2 VDD asap_7nm_pft l=7e-009 nfin=14
Xpft6 net4 net3 net1 VDD asap_7nm_pft l=7e-009 nfin=14
Xnft4 net6 net6 GND net5 asap_7nm_nft l=7e-009 nfin=14
Xnft5 Vy Vy GND net8 asap_7nm_nft l=7e-009 nfin=14
Xpft7 net1 net1 VDD VDD asap_7nm_pft l=7e-009 nfin=14
R1 Vx Vy 1k m=1
R2 Vref VCTAT 50k m=1
Runiq net8 GND 292 m=1
Xnft9 net3 net3 net7 GND asap_7nm_nft l=7e-009 nfin=14
Xnft10 net7 net7 GND GND asap_7nm_nft l=7e-009 nfin=14
Xnft11 Vy Vy GND net9 asap_7nm_nft l=7e-009 nfin=14
Xnft14 net4 net4 net6 GND asap_7nm_nft l=7e-009 nfin=14
Xnft13 Vy Vy GND GND asap_7nm_nft l=7e-009 nfin=14
Xnft15 Vy Vy GND net10 asap_7nm_nft l=7e-009 nfin=14
Xnft2 net1 net4 Vx GND asap_7nm_nft l=7e-009 nfin=14
Xnft3 net1 net4 Vx GND asap_7nm_nft l=7e-009 nfin=14
Xnft6 net1 net4 Vx GND asap_7nm_nft l=7e-009 nfin=14
Xnft7 net1 net4 Vx GND asap_7nm_nft l=7e-009 nfin=14
**** begin user architecture code
.tran 100p 2u 0
.temp 27
***.dc temp -40 150 5
.control
run
plot v(Vref)-v(VCTAT)
plot v(Vref)
plot v(VCTAT)
plot abs(v2#branch)
MEAS TRAN Vref_avg AVG v(Vref) From = 1.5u TO =2u
MEAS TRAN Vref_final find v(Vref) at = 1.5u
**** end user architecture code

```

```

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Initial Transient Solution
-----
Node                                Voltage
----                                -
vref                                0
net1                                0
vdd                                  0
vctat                                0
net4                                  0
net2                                  0
net3                                  0
net6                                  0
net5                                  0
vy                                    0
net8                                  0
vx                                    0
net7                                  0
net9                                  0
net10                                0
v2#branch                            0

Reference value : 1.99685e-06
No. of Data Rows : 20011
vref_avg      = 6.892567e-01 from= 1.500000e-06 to= 2.000000e-06
vref_final    = 6.892567e-01
ts_test       = 4.950578e-08
tstartup      = 4.942200e-10

```

Vref = 0.68925V, Tstartup = 0.495ns

Plots:

